
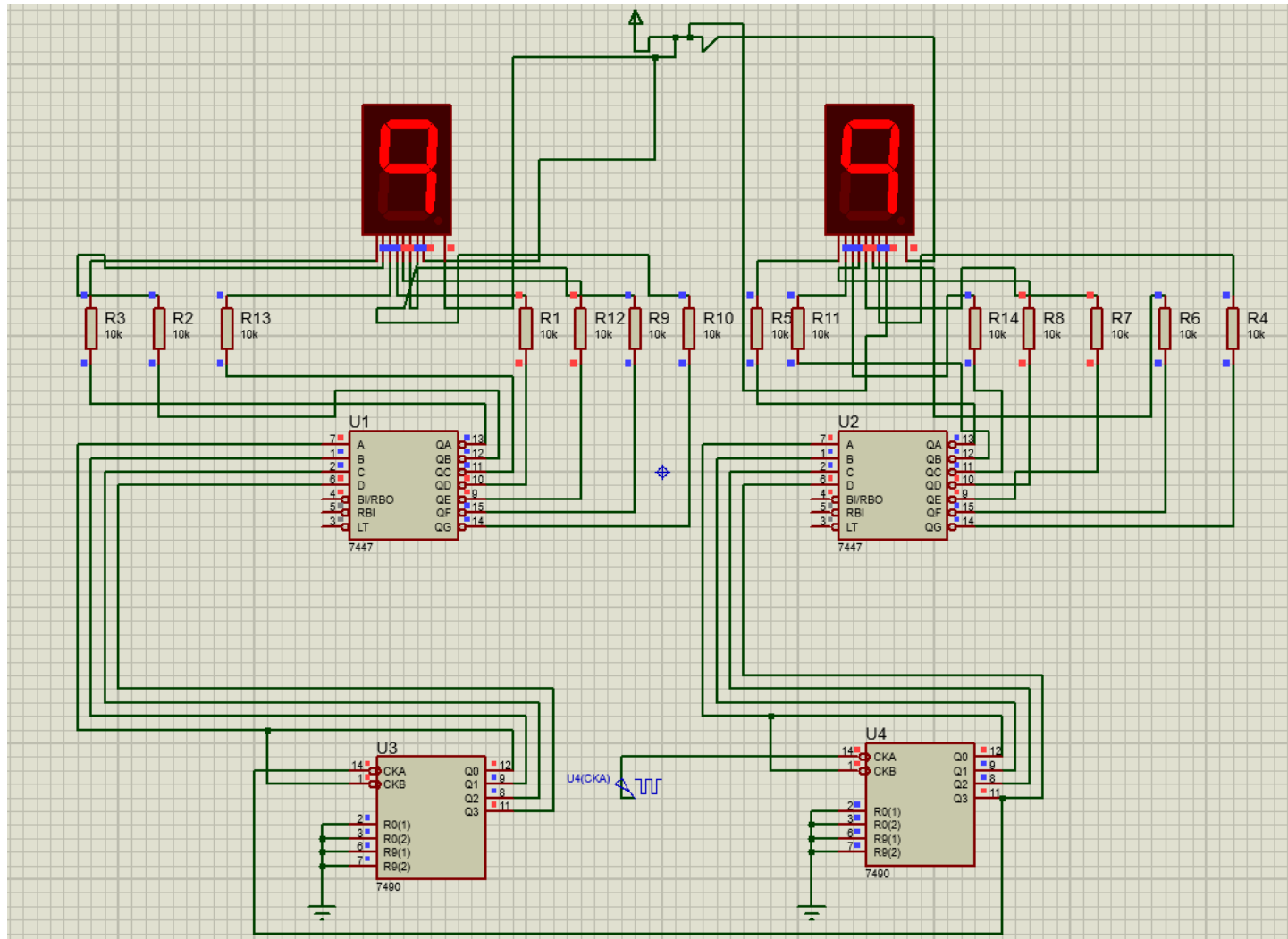


Post lab  
Exp 6  
Saja asfour  
1210737  
Sec 8

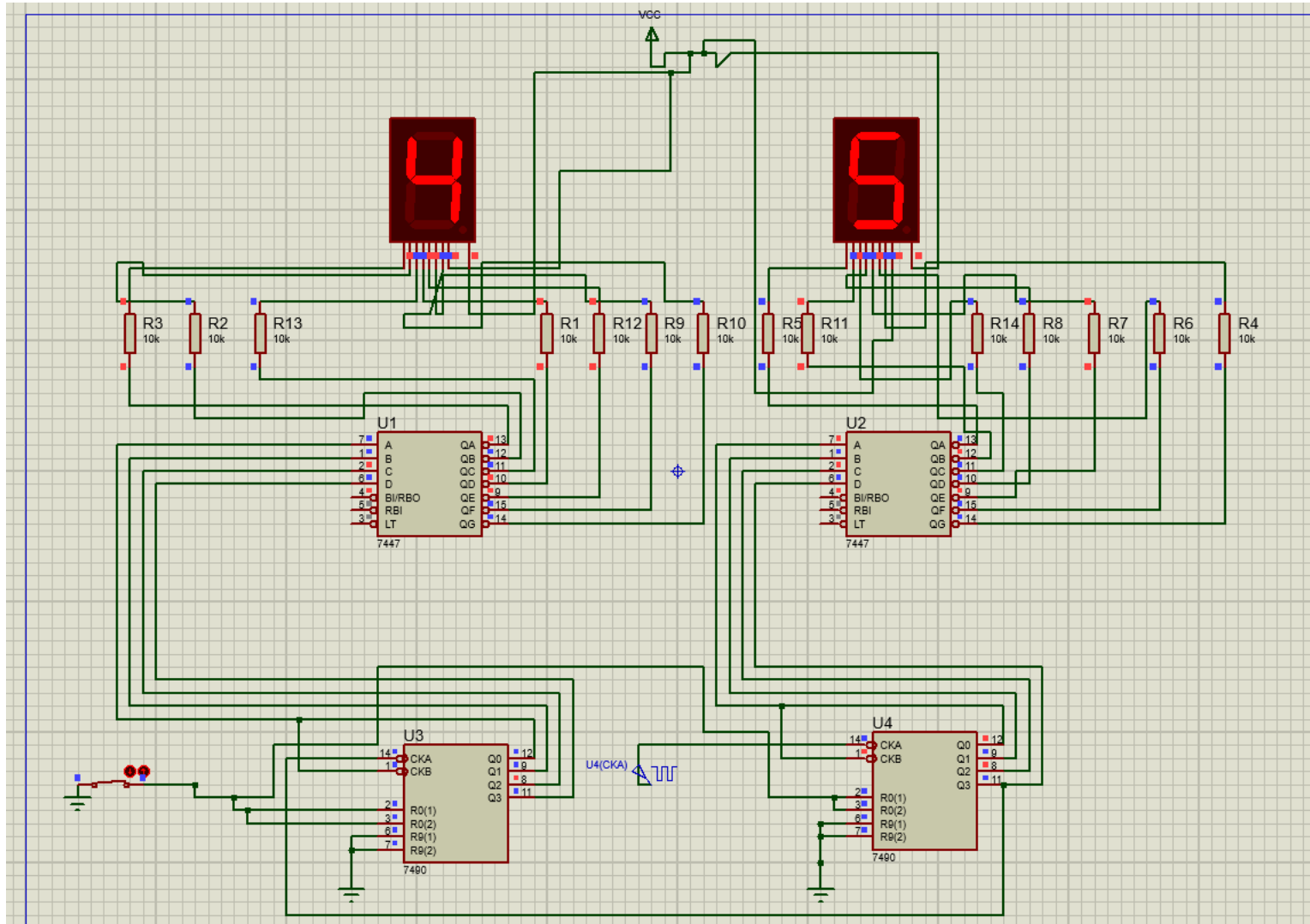1- design a two-decade counter that count from 00 to 99:



2-add additional input to your design that can be used to reset the counter



3-modifay the counter to count to 59

