

Pre lab exp 8

Encs 2110

Name: saja asfour



Id : 1210737

Sec:8

1-using quartus to build the following circuit:

 
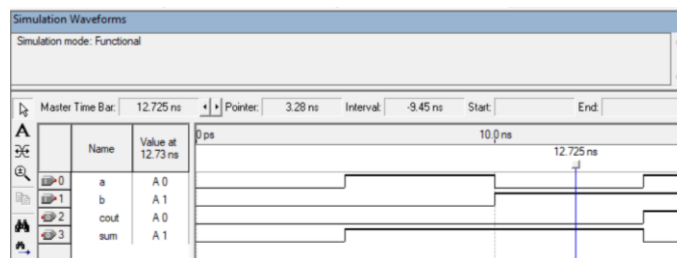
a) Build half adder on data flow:

```
1 module HA(a,b,sum,cout);  
2   input a,b;  
3   output sum,cout;  
4   assign sum=a^b;  
5   assign cout=a&b;  
6 endmodule
```



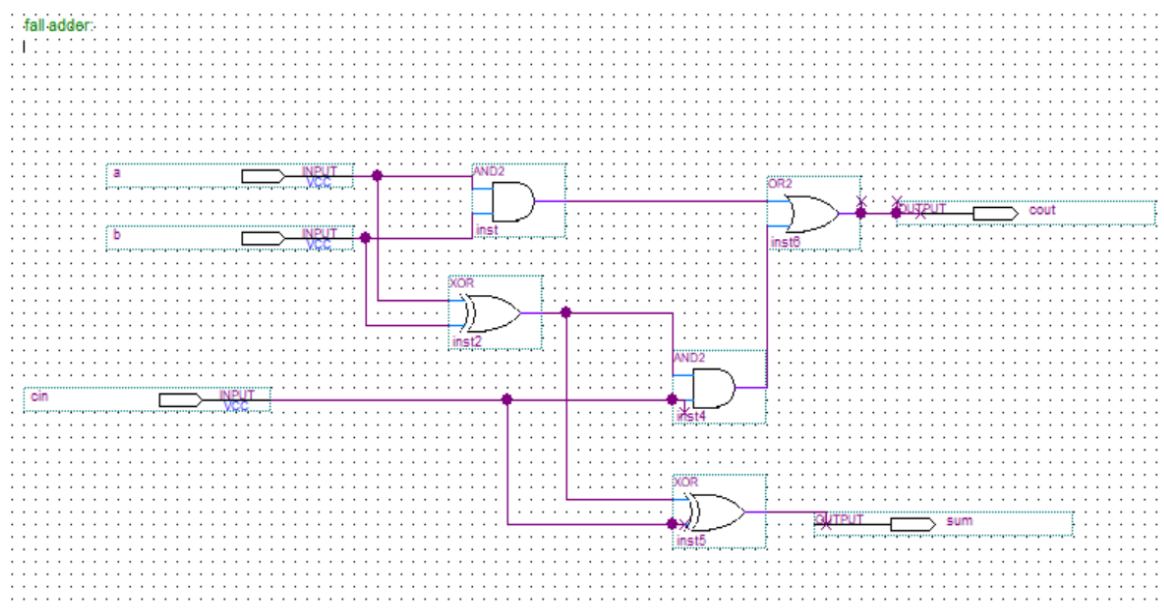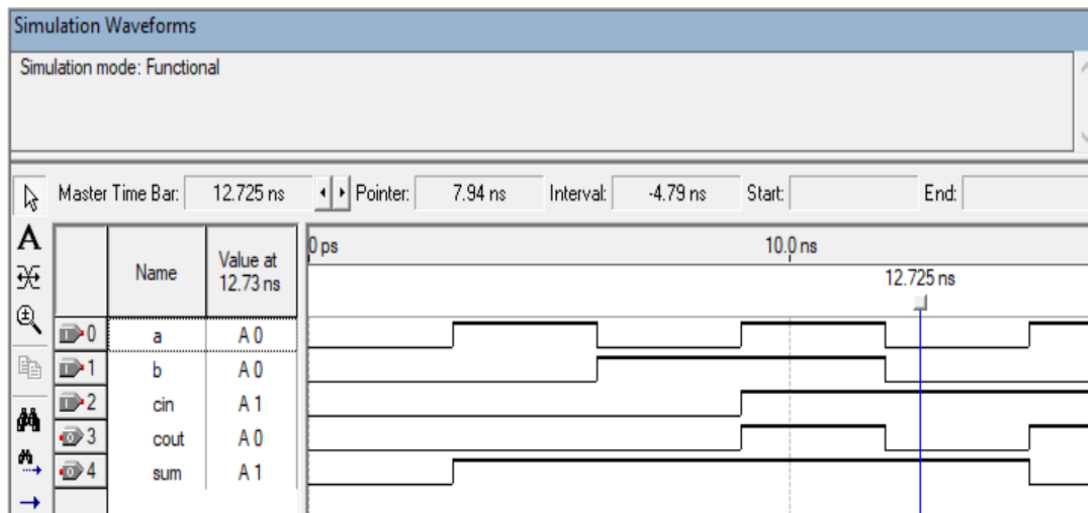b) Build the full adder using half adder structural

```
module FA(a,b,cin,sum,cout);  
  input a,b,cin;  
  output cout,sum;  
  wire s1,c1,c2;  
  HA fa0(a,b,s1,c1);  
  HA fa1(cin,s1,sum,c2);  
  or g1(cout,c2,c1);  
endmodule
```




c) Build a 2-bit counter on behavioral:

```

module counter(clk,en,rst,en_o,count);
input clk,en,rst;
output reg [1:0] count;
output reg en_o;
always @(posedge clk)
begin
    if (rst)//rst==1'b1
    begin
        count <= 0;
    end
    else if (en)//rst==1'b1
    begin
        count <= count + 1;
    end
end
end
endmodule

```

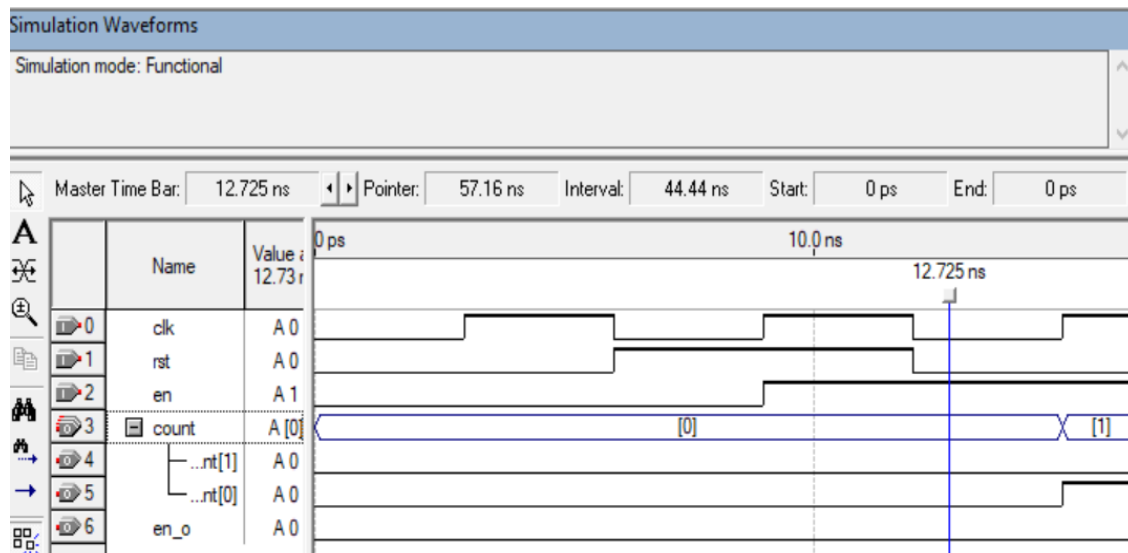


d) Build a 8*1 multiplexer on behavioral

```

module mux8(input[7:0]a,input[3:0] sel,output reg z);
always@(*)
begin
if (sel==3'b000)z=a[0];
else if(sel==3'b001) z=a[1];
else if(sel==3'b010) z=a[2];
else if(sel==3'b011) z=a[3];
else if(sel==3'b100) z=a[4];
else if(sel==3'b101) z=a[5];
else if(sel==3'b110) z=a[6];
else z=a[7];
end
endmodule

```

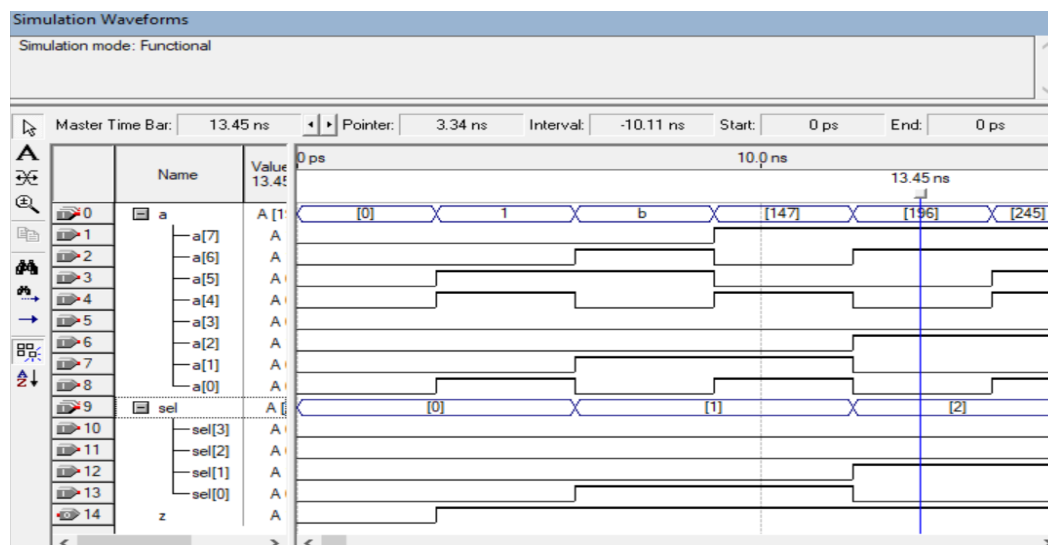

e) Build 2*4 decoder using basic gate(structural)

```

module dec2to4(en,a,b,y);
    // declare input and output ports
    input en,a,b;
    output [3:0]y;

    // supportive connections required
    // to connect nand gates
    wire enb,na,nb;

    // instantiate 4 nand gates and 3 not gates
    // make connections by referring the above logic diagram
    not n0(enb,en);
    not n1(na,a);
    not n2(nb,b);
    nand n3(y[0],enb,na,nb);
    nand n4(y[1],enb,na,b);
    nand n5(y[2],enb,a,nb);
    nand n6(y[3],enb,a,b);

endmodule

```

